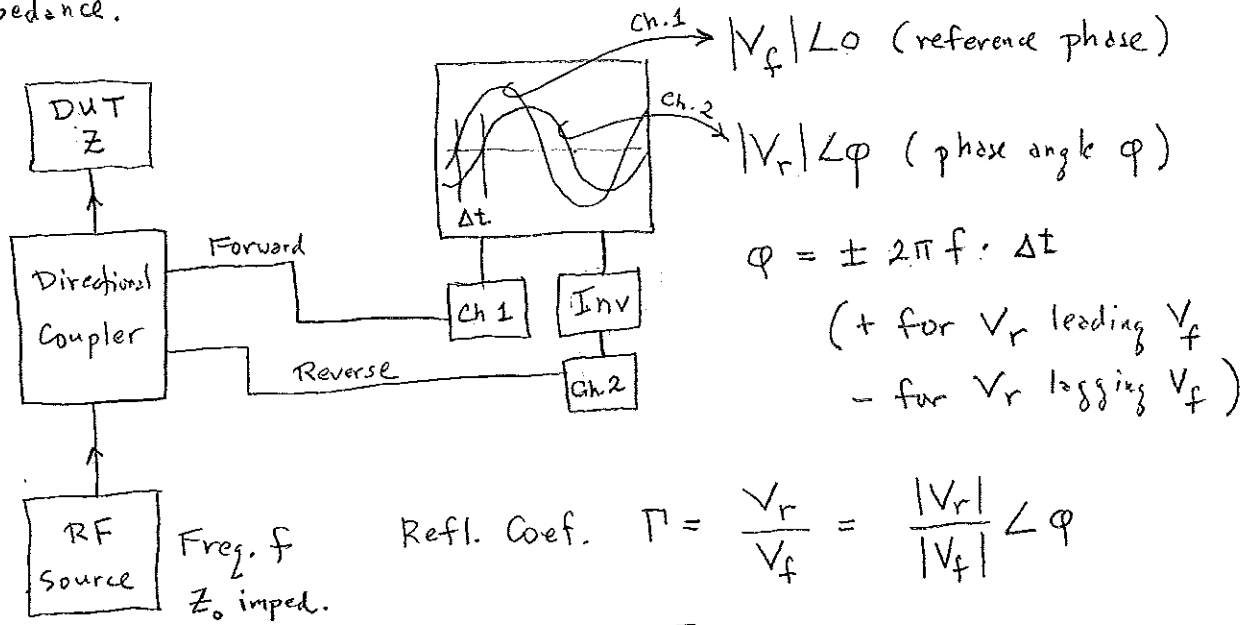


Measuring Impedance with a Directional Coupler

By attaching a directional coupler to a 2-channel oscilloscope we can measure the (complex) reflection coefficient and hence the impedance.



$$\text{Refl. Coef. } \Gamma = \frac{V_r}{V_f} = \frac{|V_r|}{|V_f|} \angle \phi$$

$$Z = Z_0 \cdot \frac{1 + \Gamma}{1 - \Gamma} \quad (\text{use complex number arithmetic})$$

See attached schematic of the directional coupler for more details.

The raw measurements made as above can be corrected (to a certain extent) for systematic errors in the cables, directional coupler, and DUT holding fixture. The correction equation has three (complex) values:

E_D = directivity, E_{RT} = reflection tracking, E_S = source match
 calculated from measured Γ for an open ($Z = \infty, \Gamma = 1$), a short ($Z = 0, \Gamma = -1$) and a matched load ($Z = Z_0, \Gamma = 0$).

Attached pages contain more details and some examples:

DUT Nominal Value	100 Ω	28 Ω	2.2 nF	100 pF	3.3 μ H	15 μ H
Adj. Z	98.4 Ω	28.0 Ω	2.14 nF	158 pF*	3.30 μ H	15.3 μ H

* - Poor est. (high reactive component)

Note: Not all resistive and reactive components are shown, but are negligible, except for 100 pF capacitor.

The Tandem Match Directional Coupler

Definitions (All quantities are phasors)

$$\text{Reflection Coefficient } \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\text{Forward Voltage } V_f = \frac{V_L}{1 + \Gamma}$$

$$\text{Reflected Voltage } V_r = \frac{\Gamma V_L}{1 + \Gamma}$$


$$\text{Forward Current } I_f = V_f / Z_L$$

$$\text{Reflected Current } I_r = -V_r / Z_L$$

if Z_L is the end of a transmission line, then these definitions coincide with the forward and reflected waves on the line.

Assumptions

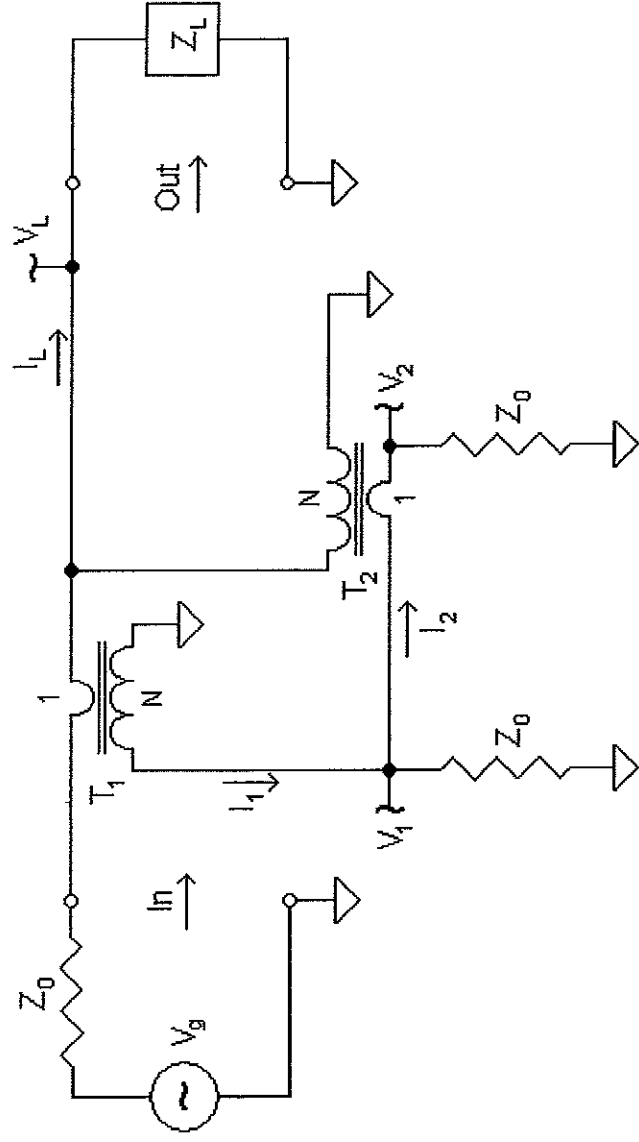- The voltage drop across the 1-turn primary of T_1 is zero.
- The current through the N-turn secondary of T_2 is zero.



From the definitions

$$V_L = V_f + V_r \text{ and } I_L = I_f - I_r \text{ since } I_L = V_L / Z_L$$

The voltage across the N-turn secondary of T_2 will be V_L , so the voltage across the 1-turn primary is

$$V_1 - V_2 = (1/N) V_L = (1/N) (V_f + V_r) \quad (*)$$

The current through the 1-turn primary of T_1 is I_L , so the current through the N-turn secondary is

$$I_1 = (1/N) I_L = (1/N) (I_f - I_r)$$

We thus get another equation

$$\begin{aligned} V_1 + V_2 &= (I_1 - I_2) Z_0 + I_2 Z_0 = I_1 Z_0 = (1/N) (I_f - I_r) Z_0 \\ &= (1/N) (V_f + V_r) (Z_0 / Z_L) \end{aligned} \quad (**)$$

Solving the simultaneous equations (*) and (**) for V_1 and V_2 gives

$$V_1 = (1/N) V_f \text{ and } V_2 = -(1/N) V_r$$

Freq (MHz): 1 — 1 MHz and a better job than 10 MHz
 Z₀ 51
 Fixture Jaws — alligator clips to BNC male adapter

DUT	V _r (mV)	V _t (mV)	Δt (ns)	V _r / V _t	φ	Measured Γ = (V _r / V _t) e ^{jφ}	Measured Z = Z ₀ (1 + Γ) / (1 - Γ)
Open	224	244	-32.8	1.08929	-0.2061	1.06623514995121 - 0.222903504583156j	-175.941779971261 - 420.471013426664j
Short	333	327	492.5	0.98198	3.0945	-0.980891859196889 + 4.62576858319917E-002j	0.46389383243539 + 1.20178222831252j
Match.	270	31.9	-200	0.11815	-1.2566	3.65097856317068E-002 - 0.1123665566184501j	53.4445587464686 - 12.18068622122212j
100 Ω	254	100.5	-67.15	0.39567	-0.4219	0.360971484103398 - 0.162030169328327j	98.9752091909042 - 38.027267853858j
28 Ω	285	70	-501	0.24561	-3.1479	-0.245609186876946 + 1.54322834241797E-003j	30.8875169748567 + 0.101453279581757j
2.2 nF	259	294	-210	1.13514	-1.3195	0.282296628673619 - 1.09947277749736j	-8.53575714858465 - 65.0523334534211j
100 pF	225	245	-47.95	1.08889	-0.3013	1.03984295518855 - 0.323118617368963j	-89.3419425769474 - 310.945697026604j
3.3 μH	295	258	361	0.87458	2.2682	-0.561698930574775 + 0.670356595785804j	4.15158064626185 + 23.673721695274j
15 μH	234	223	120	0.95299	0.7540	0.694700871431516 + 0.652367541120075j	9.02516064874257 + 128.262621126263j

↑ Nominal values

Measured on scope

↑

$\Gamma = |\Gamma| e^{j\phi}$

$\phi = \angle V_r = \angle \Gamma$

$\frac{|V_r|}{|V_t|} = |\Gamma|$

$\Gamma = |\Gamma| \cos \phi + j |\Gamma| \sin \phi$


↑

$Z = Z_0 \frac{1 + \Gamma}{1 - \Gamma}$

Not adjusted for errors

These measured values Γ_M of the reflection coefficient must be adjusted for some systematic errors due to imperfections.

DUT	Adjusted Γ	Adjusted Z	R (Ω)	C (F)	L (H)	Return Loss (dB)	VSWR
Open	1	Infinite	Infinite			0	Infinite
Short	-1	0	0			0	Infinite
Match	0	51	51			Infinite	1
100 Ω	0.317289520258091-9.06874490039249E-003j	98.3781160815808-1.98425550601946j	98.38	8.02E-08		9.967	1.93
28 Ω	-0.286387762090108+7.19880980765342E-002j	28.0442576560812+4.42342965334757j	28.04		7.04E-07	10.595	1.84
2.2 nF	0.347301610226974-0.897893984336017j	3.02830709731409-74.3248224396678j	3.03	2.14E-09		0.330	52.65
100 pF	0.982774819366333-9.80738374220247E-002j	126.199772352475-1008.91027121942j	126.20	1.58E-10		0.108	161.03
3.3 μ H	-0.695190616175597+0.678136339335522j	0.869615073132535+20.7496847566634j	0.87		3.30E-06	0.254	68.36
15 μ H	0.557606823102455+0.823514612802693j	0.636024243488917+96.1204257483279j	0.64		1.53E-05	0.048	365.03

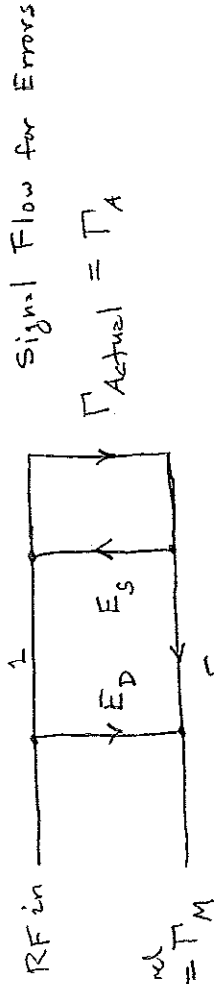

$$\Gamma_M = E_D + E_{RT} \left[\frac{\Gamma_A}{1 - E_S \Gamma_A} \right]$$

(complex values)

Solving for Γ_A :

$$\Gamma_A = \frac{\Gamma_M - E_D}{E_{RT} + E_S (\Gamma_M - E_D)}$$

Correction Equation

- O - M 1.0297253643195-0.110537938398655j
- O - S 2.0471270091481-0.269161190415148j
- M - S 1.0174016448286-0.158623252016493j
- E_D 3.65097856317068E-002-0.112365566184501j
- E_S 2.88177561549078E-003+2.38680724521074E-002j
- E_{RT} 1.02411959935155-0.134796952464542j

- O = Measured Γ_M for open $Z = \infty$, $\Gamma_A = 1$
- S = Measured Γ_M for short $Z = 0$, $\Gamma_A = -1$
- M = Measured Γ_M for matched load $Z_0 = 51 \Omega$, $\Gamma_A = 0$

$$E_D = M$$

$$E_S = \frac{(O - M) - (M - S)}{(O - S)}$$

$$E_{RT} = 2(M - S) \left(\frac{O - M}{O - S} \right)$$

Estimated from three known DUTs. Use in correction equation

Corrected Γ value