



From the definitions

$$V_L = V_1 + V_2 \quad \text{and} \quad I_L = I_1 - I_2, \quad \text{since} \quad I_L = V_L / Z_L$$

The voltage across the N-turn secondary of T_2 will be V_L , so the voltage across the 1-turn primary is

$$V_1 - V_2 = (1/N) V_L = (1/N) (V_1 + V_2) \quad (*)$$

The current through the 1-turn primary of T_1 is I_1 , so the current through the N-turn secondary is

$$I_1 = (1/N) I_L = (1/N) (I_1 - I_2)$$

We thus get another equation

$$\begin{aligned} V_1 + V_2 &= (I_1 - I_2) Z_0 + I_2 Z_0 = I_1 Z_0 = (1/N) (I_1 - I_2) Z_0 \\ &= (1/N) (V_1 + V_2) (Z_0 / Z_L) \end{aligned} \quad (**)$$

Solving the simultaneous equations (*) and (**) for V_1 and V_2 gives

$$V_1 = (1/N) V_L \quad \text{and} \quad V_2 = -(1/N) V_L$$

The Tandem Match Directional Coupler

Definitions (All quantities are phasors)

$$\text{Reflection Coefficient } \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\text{Forward Voltage } V_f = \frac{V_L}{1 + \Gamma}$$

$$\text{Reflected Voltage } V_r = \frac{\Gamma V_L}{1 + \Gamma}$$

$$\text{Forward Current } I_f = V_f / Z_L$$

$$\text{Reflected Current } I_r = -V_r / Z_L$$

If Z_L is the end of a transmission line, then these definitions coincide with the forward and reflected waves on the line.

Assumptions

The voltage drop across the 1-turn primary of T_1 is zero.

The current through the N-turn secondary of T_2 is zero.